



# **Aula XII – Modelagem de Circuitos Sequenciais em VHDL**



## Tópicos da aula

- **Blocos construtivos básicos**
- **Inferência de flip-flops**
- **Registradores**
- **Contadores**
- **Máquinas de Estado**




## Circuitos Sequenciais

- ☐ São aqueles cujas saídas dependem do estado atual e passado das entradas
- ☐ Exemplos:
  - ☐ Registradores
  - ☐ Contadores
  - ☐ Máquinas de Estado


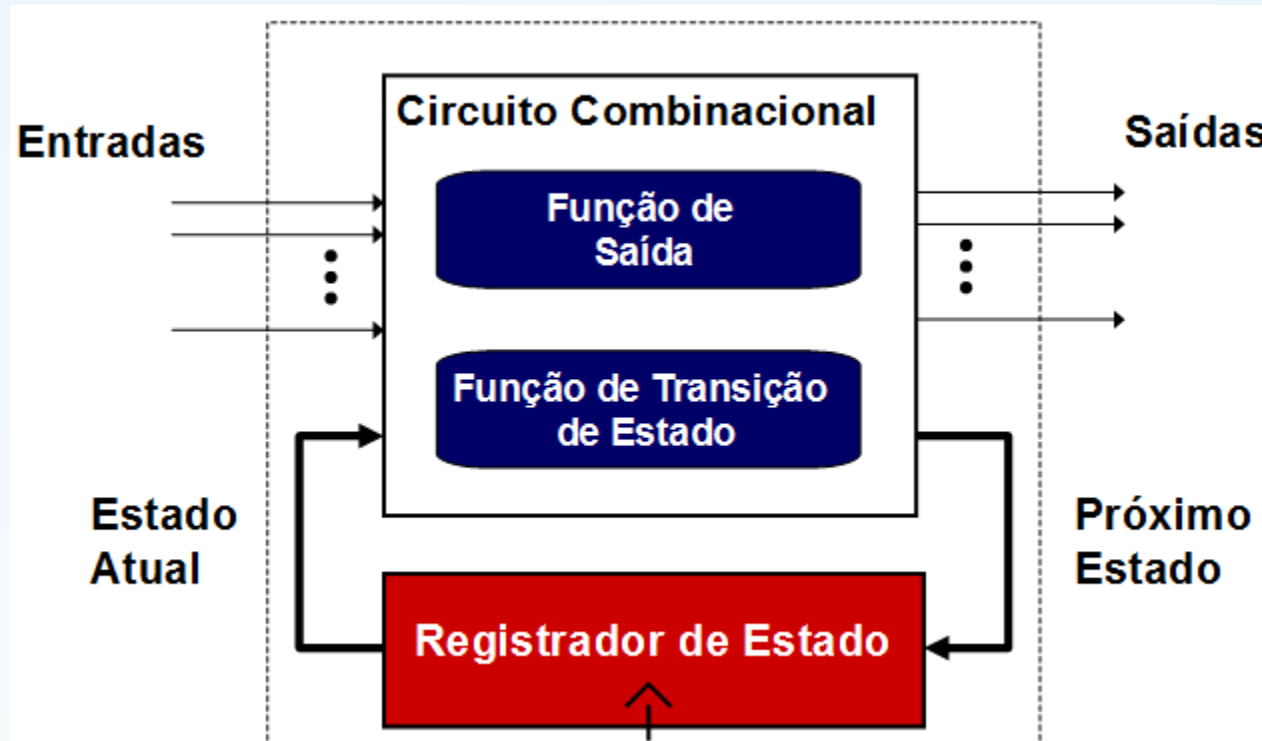
## Arquitetura genérica de um circuito sequencial







Universidade Federal  
de Santa Catarina

## Blocos construtivos básicos

### ❑ Latches

 


### ❑ Flip-flops

 




## Latch transparente

 


```
ENTITY latch_d IS
  PORT (d      : IN  BIT;  -- data input
        ena    : IN  BIT;  -- enable
        q      : OUT BIT); -- data output
END latch_d;
```
 
```
-----
ARCHITECTURE behavior OF latch_d IS
BEGIN
  PROCESS (d,ena)
  BEGIN
    IF (ena = '1') THEN
      Q <= D;
    END IF;
  END PROCESS;
END behavior;
```






## Latch com clear

 

```
ENTITY latch_d_clear IS
    PORT (d      : IN  BIT;  -- data input
          ena    : IN  BIT;  -- enable
          clrn   : IN  BIT;  -- clear
          q      : OUT BIT); -- data output
END latch_d_clear;


-----

 ARCHITECTURE behavior OF latch_d_clear IS
BEGIN
    PROCESS (d,ena,clrn)
    BEGIN
        IF (clrn = '0') THEN
            Q <= '0';
        ELSIF (ena = '1') THEN
            Q <= D;
        END IF;
    END PROCESS;
END behavior;
```






## Flip-flop tipo D

 

```
ENTITY ff_d IS
  PORT (d   : IN  BIT; -- data input
        clk : IN  BIT; -- clock
        q   : OUT BIT); -- data output
END ff_d;
```

 
```
-----
ARCHITECTURE arch_1 OF ff_d IS
BEGIN
  PROCESS
  BEGIN
    WAIT UNTIL clk='1';
    Q <= D;
  END PROCESS;
END arch_1;
```








## Flip-flop tipo D

 


```
ENTITY ff_d IS
  PORT (d    : IN  BIT;  -- data input
        clk  : IN  BIT;  -- clock
        q    : OUT BIT); -- data output
END ff_d;
```
 
```
-----
ARCHITECTURE arch_2 OF ff_d IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clk'EVENT AND clk='1') THEN
      Q <= D;
    END IF;
  END PROCESS;
END arch_2;
```






## Flip-flop tipo D

 


```
LIBRARY IEEE;  
USE IEEE.std_logic_1164.ALL;  
  
ENTITY ff_d_std_logic IS  
    PORT (d      : IN  STD_LOGIC;  -- data input  
          clk    : IN  STD_LOGIC;  -- clock  
          q      : OUT STD_LOGIC); -- data output  
END ff_d_std_logic;
```
 
```
-----  
ARCHITECTURE arch_1 OF ff_d_std_logic IS  
BEGIN  
    PROCESS (clk)  
    BEGIN  
        IF rising_edge (clk) THEN  
            Q <= D;  
        END IF;  
    END PROCESS;  
END arch_1;
```






## Flip-flop tipo D com clear

 

```
ENTITY ff_d_clear IS
    PORT (d : IN BIT; -- data input
          clk : IN BIT; -- clock
          clrn: IN BIT; -- clear
          q : OUT BIT); -- data output
END ff_d_clear;

-----

 ARCHITECTURE arch_1 OF ff_d_clear IS
BEGIN
    PROCESS(clk, clrn)
    BEGIN
        IF (clrn='0') THEN
            Q <= '0';
        ELSIF (clk'EVENT AND clk='1') THEN
            Q <= D;
        END IF;
    END PROCESS;
END arch_1;
```







## Inferência de flip-flops

### ❑ Quando flip-flops serão inferidos para reg1.vhd?


```
ENTITY reg1 IS
    PORT ( d      : IN  BIT;
           clk     : IN  BIT;
           q      : OUT BIT);
END reg1;

-----
ARCHITECTURE arch_1 OF reg1 IS
    SIGNAL a, b : BIT;
BEGIN
    PROCESS (clk)
    BEGIN
        IF (clk'EVENT AND clk='1') THEN
            a <= d;
            b <= a;
            q <= b;
        END IF;
    END PROCESS;
END arch_1;
```


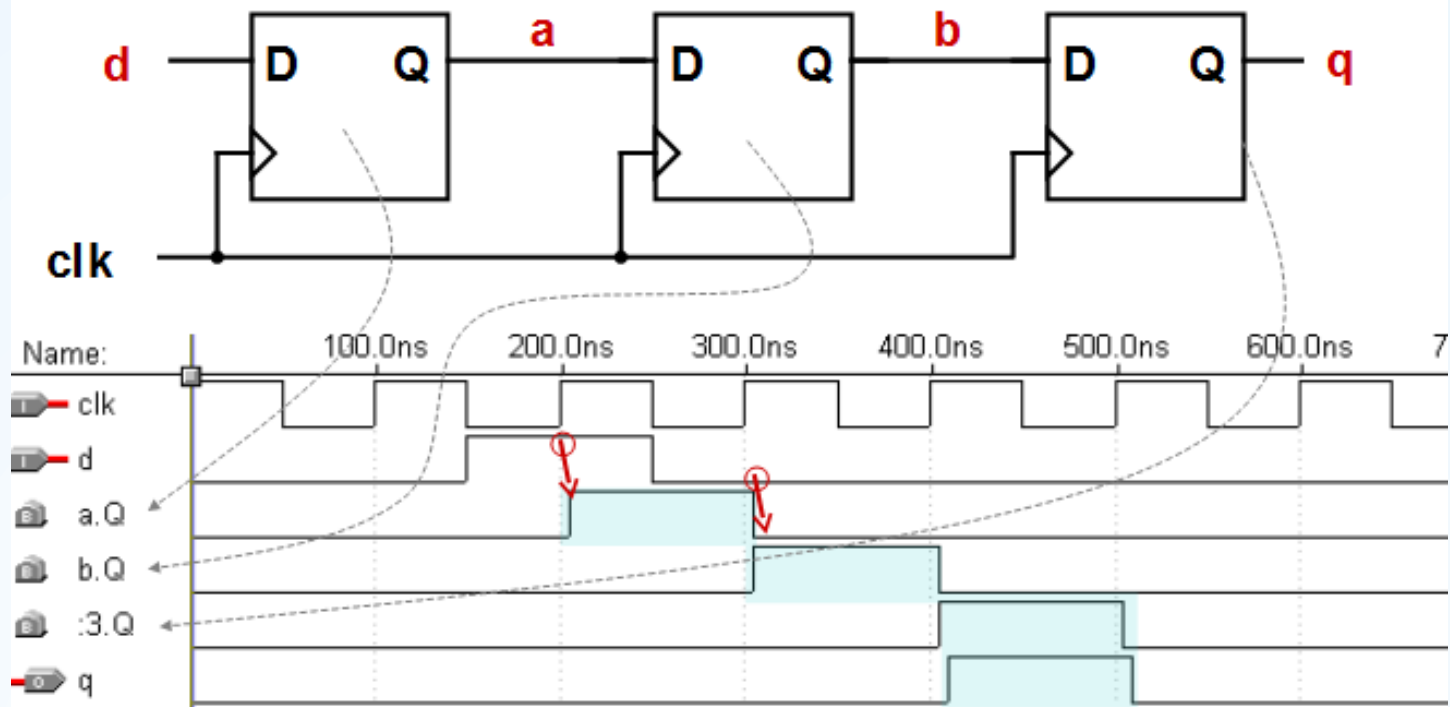
## Inferência de flip-flops

□ Quando flip-flops serão inferidos reg1.vhd?





## Inferência de flip-flops

### ❑ Quando flip-flops serão inferidos para reg2.vhd?


```
ENTITY reg2 IS
  PORT ( d    : IN  BIT;
         clk  : IN  BIT;
         q    : OUT BIT);
END reg1;

-----
ARCHITECTURE arch_1 OF reg2 IS
  SIGNAL a, b : BIT;
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clk'EVENT AND clk='1') THEN
      a <= d;
      b <= a;
    END IF;
  END PROCESS;
  q <= b;
END arch_1;
```


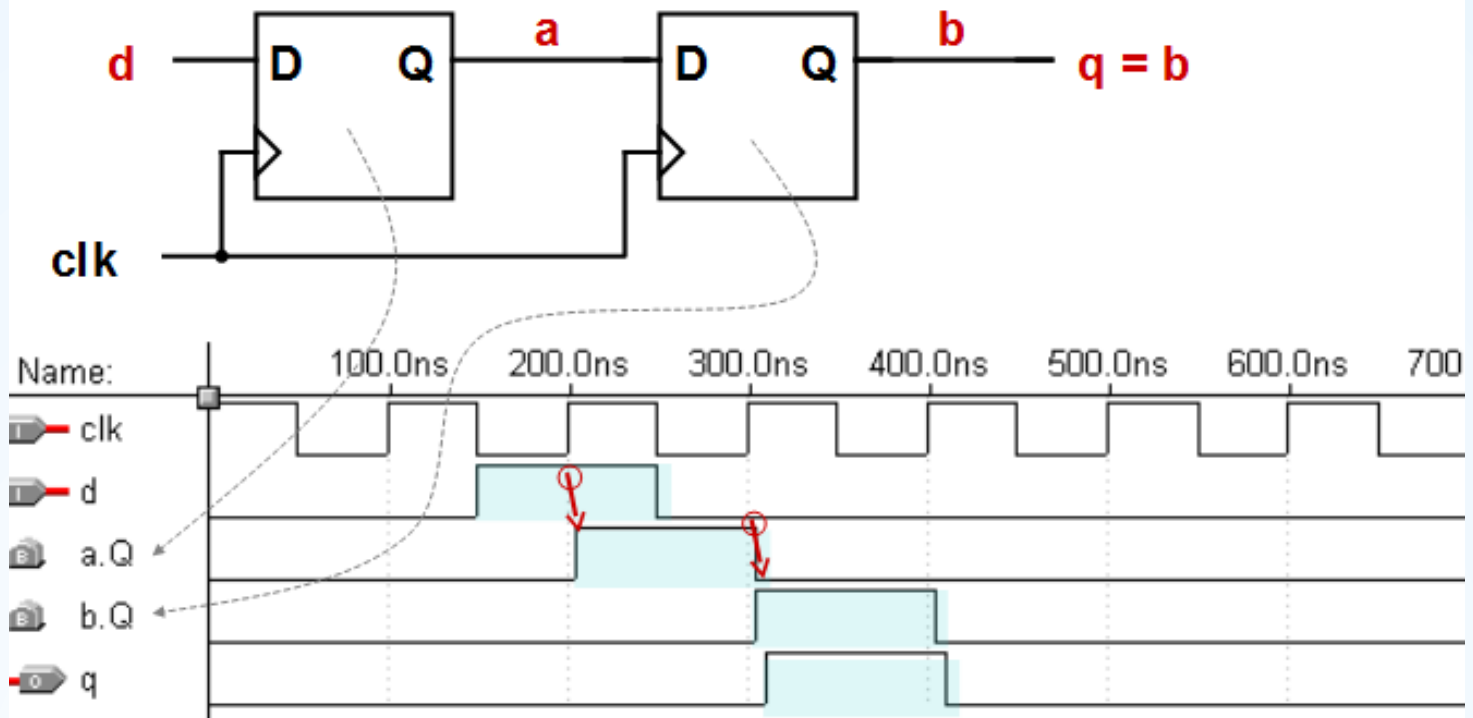
## Inferência de flip-flops

□ Quando flip-flops serão inferidos reg2.vhd?







## Inferência de flip-flops

### ❑ Quando flip-flops serão inferidos para reg3.vhd?


```
ENTITY reg3 IS
  PORT ( d    : IN  BIT;
         clk  : IN  BIT;
         q    : OUT BIT);
END reg1;

-----
ARCHITECTURE arch_1 OF reg3 IS
BEGIN
  PROCESS (clk)
    VARIABLE a, b : BIT;
  BEGIN
    IF (clk'EVENT AND clk='1') THEN
      a := d;
      b := a;
      q <= b;
    END IF;
  END PROCESS;
END arch_1;
```


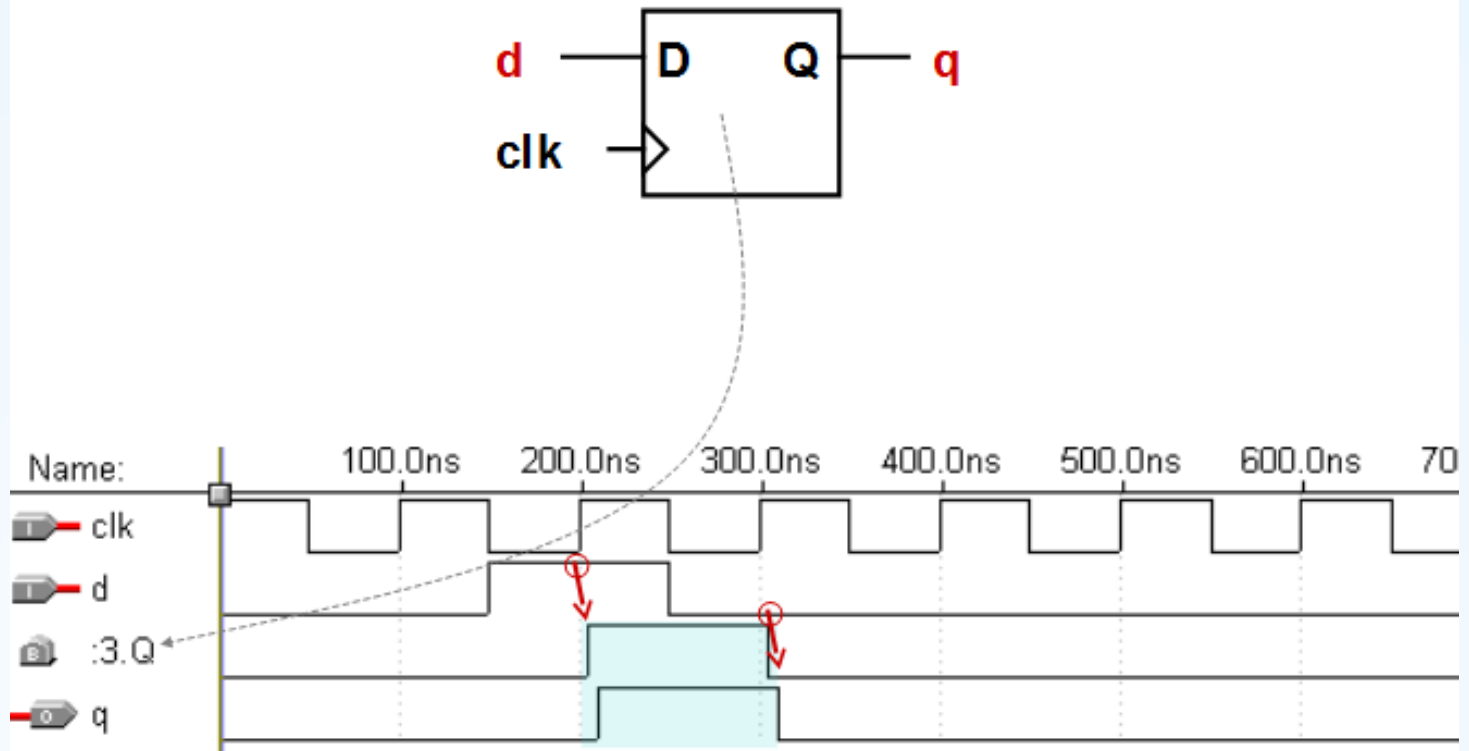
## Inferência de flip-flops


□ Quando flip-flops serão inferidos reg3.vhd?





## Registradores
 
### □ Registrador Paralelo-Paralelo de W bits





## Registradores

### ❑ Registrador Paralelo-Paralelo de W bits

```
ENTITY reg_pp_Wbits IS
    GENERIC (W : NATURAL := 4);
    PORT (d : IN BIT_VECTOR(W-1 DOWNT0 0); -- data input
          clk : IN BIT; -- clock
          clrn : IN BIT; -- clear
          ena : IN BIT; -- enable
          q : OUT BIT_VECTOR(W-1 DOWNT0 0)); -- data output
END reg_pp_Wbits;


ARCHITECTURE arch_1 OF reg_pp_Wbits IS
BEGIN
    PROCESS (clk, clrn)
    BEGIN
        IF (clrn='0') THEN
            q <= (OTHERS => '0');
        ELSIF (clk'EVENT AND clk='1') THEN
            IF (ena='1') THEN
                q <= d;
            END IF;
        END IF;
    END PROCESS;
END arch_1;
```

**Igual ao  
flip-flop  
tipo D com  
clear e  
enable**



## Registradores
 
### ❑ Registrador Paralelo-Paralelo de W bits






## Contadores

### ❑ Incrementador de W bits

❑ Aplicação típica: Program Counter (PC)

CLRn	Ena	Load	Qf
0	X	X	0
1	0	X	Qa
	1	1	D
		0	Qa+1

CLRn é assíncrono

 



## Contadores

### ❑ Incrementador de W bits – Entidade

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.std_logic_unsigned.ALL;

ENTITY counter_Wbits IS
    GENERIC (W : NATURAL := 4);
    PORT (d      : IN  STD_LOGIC_VECTOR(W-1 DOWNT0 0); -- data input
          clk    : IN  BIT;      -- clock
          clrn   : IN  BIT;      -- clear
          ena    : IN  BIT;      -- enable
          load   : IN  BIT;      -- load
          q      : BUFFER STD_LOGIC_VECTOR(W-1 DOWNT0 0)); -- data
    output
END counter_Wbits;
```



## Contadores

### ❑ Incrementador de W bits – Arquitetura


```
ARCHITECTURE arch_1 OF counter_Wbits IS
BEGIN
  PROCESS (clk, clrn)
  BEGIN
    IF (clrn='0') THEN
      q <= (OTHERS => '0');
    ELSIF (clk'EVENT AND clk='1') THEN
      IF (ena='1') THEN
        IF (load='1') THEN
          q <= d;
        ELSE
          q <= q+1;
        END IF;
      END IF;
    END IF;
  END PROCESS;
END arch_1;
```





## Contadores

### Incrementador de W bits

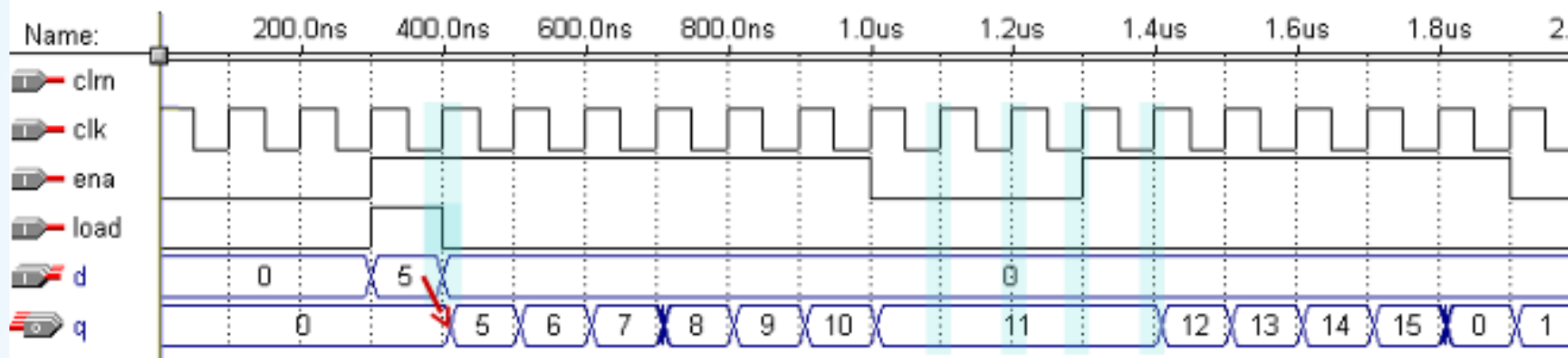



## **FIM AULA XIII**